2025/10/02 08:30 1/3 Lab Work 2 (Part 2)


## Lab Work 2 (Part 2)

### **Adders and Comparators**

One of the most useful combinational logic circuit is an adder. It is the core component of any Arithmetic Unit - used in binary multipliers and even floating-point arithmetic units. Meanwhile, a comparator is useful as a decision making circuitry - it usually compares the magnitude of two binary values.
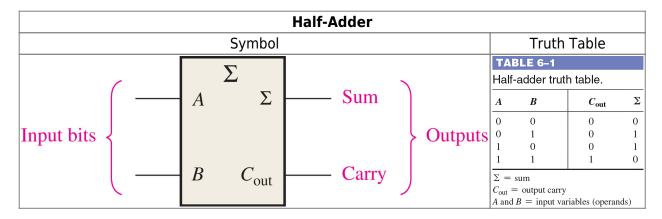
#### Half-Adder


A half-adder sums two 1-bit values and provides two 1-bit values (sum and carry).



**Disclaimer**: The images above are extracted from resources available for Digital Fundamentals 11th Edition (Global Edition)
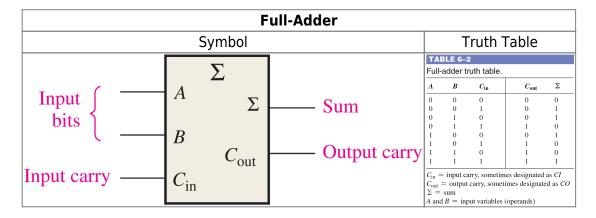
### **Full-Adder**

A full-adder sums three 1-bit values and provides two 1-bit values (sum and carry).



**Disclaimer**: The images above are extracted from resources available for Digital Fundamentals 11th Edition (Global Edition)

## **Comparator**

There are three possible output bits of a comparator (depending on application requirement): equality (==), less than (<) and greater than (>).

<b>Comparator Output</b>	Description			
F()(==)	Output is at logic HI when the first value is exactly the same as the second value			
LT (<)	Output is at logic HI when the first value is less than the second value			
GT (>)	Output is at logic HI when the first value is greater then the second value			

Truth Table for a 1-bit Comparator:

Α	В	ΕQ	LT	GΤ
0	0	1	0	0
0	1	0	1	0
1	0	0	0	1
1	1	1	0	0

Note: A 2-bit comparator cannot be built by simply cascading two 1-bit logic circuits.

# **Things To Do**

**THING 1** Build a 1-bit half-adder circuit and verify.

**THING 2** Build a 1-bit full-adder circuit using 2×1-bit half-adders. Verify. *Trivia: What is the least number of ICs (of 2-input logic gates) needed to implement this?* 

THING 3 (Optional?) Build a 2-bit adder and verify.

**THING 4** (Optional?) Construct a truth table for 1-bit subtractor. Build the circuit and verify.

**THING 5** (Optional?) Build a 4-bit ripple carry adder and verify.

**THING 6** (Optional?) Build a 4-bit carry look ahead (CLA) adder and verify.

**THING 7** Construct a truth table for 2-bit comparator (3 outputs). Get the Boolean expression for each output. Build the circuit and verify.

**THING 8** (Optional?) Build a 4-bit comparator (3 outputs) and verify.

ask your instructor for more...

From:

http://azman.unimap.edu.my/dokuwiki/ - Azman @UniMAP

Permanent link:

http://azman.unimap.edu.my/dokuwiki/doku.php?id=archive:pgt104lab01b

Last update: 2020/09/13 18:58

