

NMK20603

Computer Architecture

Describing Combinational Logic (cont.)

Codes so far:


- ✓ mux21_1b, mux21_1b_tb
- ✓ mux41_1b, mux41_1b_tb
- ✓ mux21_2b, mux21_2b_tb
- ✓ mux41_2b, mux41_2b_tb
- ✓ dmux21, dmux21_tb (only this matters)

Homework?

⇒ dmux41

⇒ dmux41_tb

Let's do
arithmetic!
⇒ 1-bit Add

 

iC	iP	iQ	oC	oS
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Get SOP equation!

Describe:

add_1b

```
module add_1b (iC,iP,iQ,oC,oS);  
input iC,iP,iQ;  
output oC, oS;  
wire oC, oS, tP, tG, tP1, tP2, tS1, tS2, tX;  
// just to show order DOES NOT matter  
assign oS = tS1 | tS2; // iC ^ tP;  
assign oC = tG | tX;  
assign tG = iP & iQ;  
assign tP1 = iP & ~iQ;  
assign tP2 = ~iP & iQ;  
assign tP = tP1 | tP2; // iP ^ iQ;  
assign tS1 = iC & ~tP;  
assign tS2 = ~iC & tP;  
assign tX = iC & tP;  
endmodule
```

Describe:


add_1b_tb

```

module add_1b_tb ();
reg dC,dP,dQ;
wire mC,mS;
reg cC,cS;
integer loop,ecnt;
initial begin
    ecnt = 0;
    for (loop=0;loop<8;loop=loop+1) begin
        {dC,dP,dQ} = loop;
        #5;
        {cC,cS} = dC+dP+dQ; // or, do a truth table!
        if (mC!=cC||mS!=cS) begin
            ecnt = ecnt + 1;
        end
        #5;
    end
    if (ecnt==0) begin
        $display("-- Module add_1b verified!");
    end
    else begin
        $display("*** Module add_1b with error(s)! (%d)",ecnt);
    end
    $stop;
end
add_1b dut (dC,dP,dQ,mC,mS);
endmodule

```

4-bit Add

 


Equation?

⇒ Check on-paper

4-digit Addition!

4-bit Add

 

Ripple-Carry Adder!

Describe:

add_4b

```
module add_4b (iC,iP,iQ,oC,oS);  
  input iC;  
  input[3:0] iP,iQ;  
  output oC;  
  output[3:0] oS;  
  wire oC;  
  wire[3:0] oS;  
  wire[2:0] tC;  
  add_1b bit0 (iC,iP[0],iQ[0],tC[0],oS[0]);  
  add_1b bit1 (tC[0],iP[1],iQ[1],tC[1],oS[1]);  
  add_1b bit2 (tC[1],iP[2],iQ[2],tC[2],oS[2]);  
  add_1b bit3 (tC[2],iP[3],iQ[3],oC,oS[3]);  
endmodule
```

Extra:

⇒ CLA?

Describe:


add_4b_tb

```

module add_4b_tb ();
reg dC;
reg[3:0] dP,dQ;
wire mC;
wire[3:0] mS;
reg cC;
reg[3:0] cS;
integer loop,ecnt;
initial begin
    ecnt=0;
    for (loop=0;loop<512;loop=loop+1) begin
        {dC,dP,dQ} = loop;
        #5;
        {cC,cS} = dP + dQ + dC;
        if (mC!=cC||mS!=cS) begin
            ecnt = ecnt + 1;
        end
        #5;
    end
    if (ecnt==0) begin
        $display("-- Module add_4b verified!");
    end
    else begin
        $display("*** Module add_4b with error(s)! (%d)",ecnt);
    end
    $stop;
end
add_4b dut (dC,dP,dQ,mC,mS);
endmodule

```

1-bit Subtract

 

iB	iP	iQ	oB	oD
0	0	0	0	0
0	0	1	1	1
0	1	0	0	1
0	1	1	0	0
1	0	0	1	1
1	0	1	1	0
1	1	0	0	0
1	1	1	1	1

Get SOP equation!

Homework:

⇒ sub_1b, sub_1b_tb

⇒ sub_4b, sub_4b_tb