

NMK20603

# Computer Architecture

# Describing Combinational Logic (cont.)

Codes so far:


- ✓ mux21\_1b, mux21\_1b\_tb
- ✓ mux41\_1b, mux41\_1b\_tb
- ✓ mux21\_2b, mux21\_2b\_tb
- ✓ mux41\_2b, mux41\_2b\_tb
- ✓ dmux21, dmux21\_tb (only this matters)

# Homework?

⇒ dmux41

⇒ dmux41\_tb

Let's do  
arithmetic!  
⇒ 1-bit Add

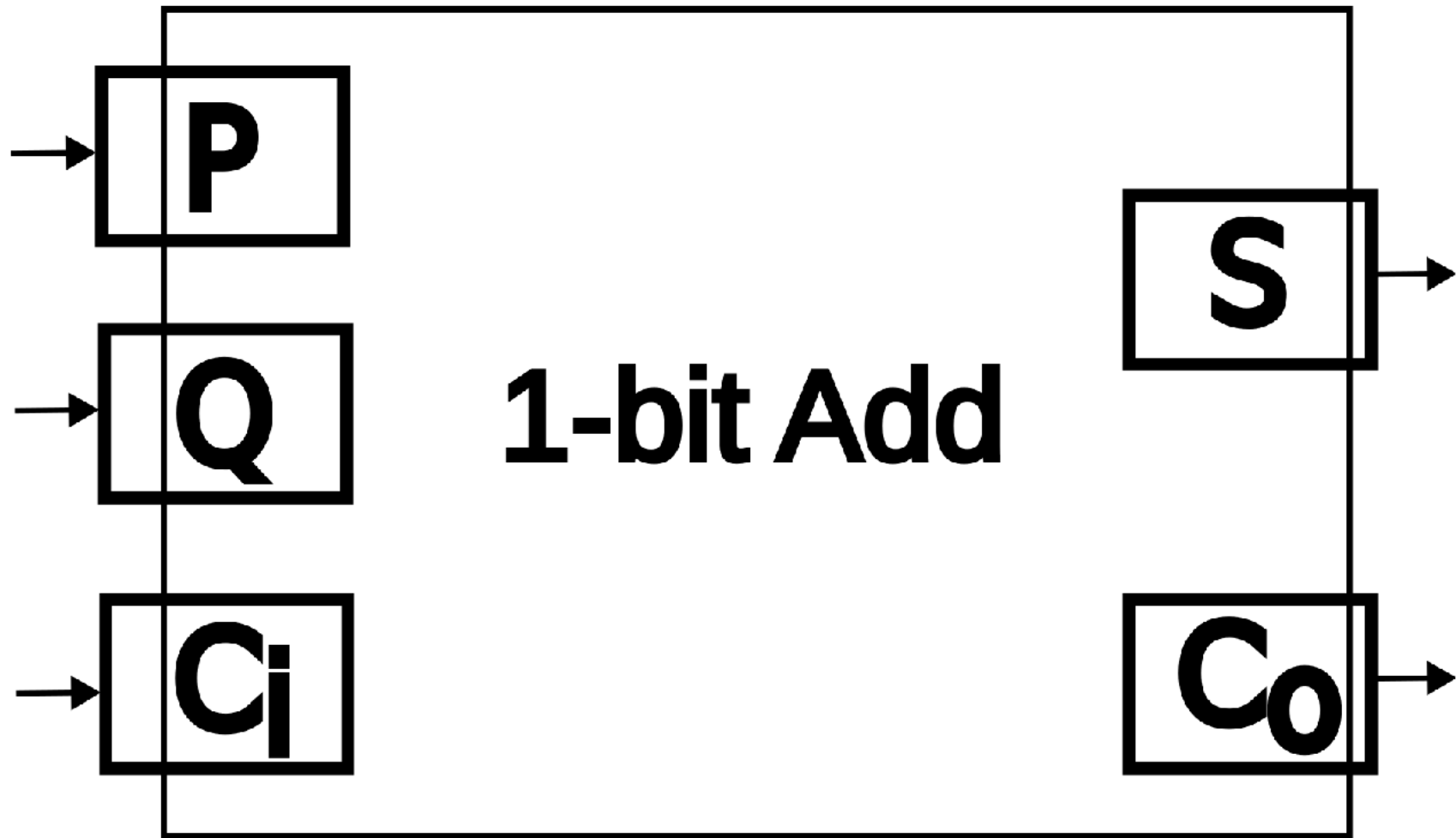

iC	iP	iQ	oC	oS
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Get SOP equation!



# Describe:

# add\_1b

```
module add_1b (iC,iP,iQ,oC,oS);
input iC,iP,iQ;
output oC, oS;
wire oC, oS, tP, tG, tP1, tP2, tS1, tS2, tX;
// just to show order DOES NOT matter
assign oS = tS1 | tS2; // iC ^ tP;
assign oC = tG | tX;
assign tG = iP & iQ;
assign tP1 = iP & ~iQ;
assign tP2 = ~iP & iQ;
assign tP = tP1 | tP2; // iP ^ iQ;
assign tS1 = iC & ~tP;
assign tS2 = ~iC & tP;
assign tX = iC & tP;
endmodule
```

# Describe:


# add\_1b\_tb

```

module add_1b_tb ();
reg dC,dP,dQ;
wire mC,mS;
reg cC,cS;
integer loop,ecnt;
initial begin
    ecnt = 0;
    for (loop=0;loop<8;loop=loop+1) begin
        {dC,dP,dQ} = loop;
        #5;
        {cC,cS} = dC+dP+dQ; // or, do a truth table!
        if (mC!=cC||mS!=cS) begin
            ecnt = ecnt + 1;
        end
        #5;
    end
    if (ecnt==0) begin
        $display("-- Module add_1b verified!");
    end
    else begin
        $display("*** Module add_1b with error(s)! (%d)",ecnt);
    end
    $stop;
end
add_1b dut (dC,dP,dQ,mC,mS);
endmodule

```

# 4-bit Add

 


Equation?

⇒ Check on-paper

4-digit Addition!

## 4-bit Add

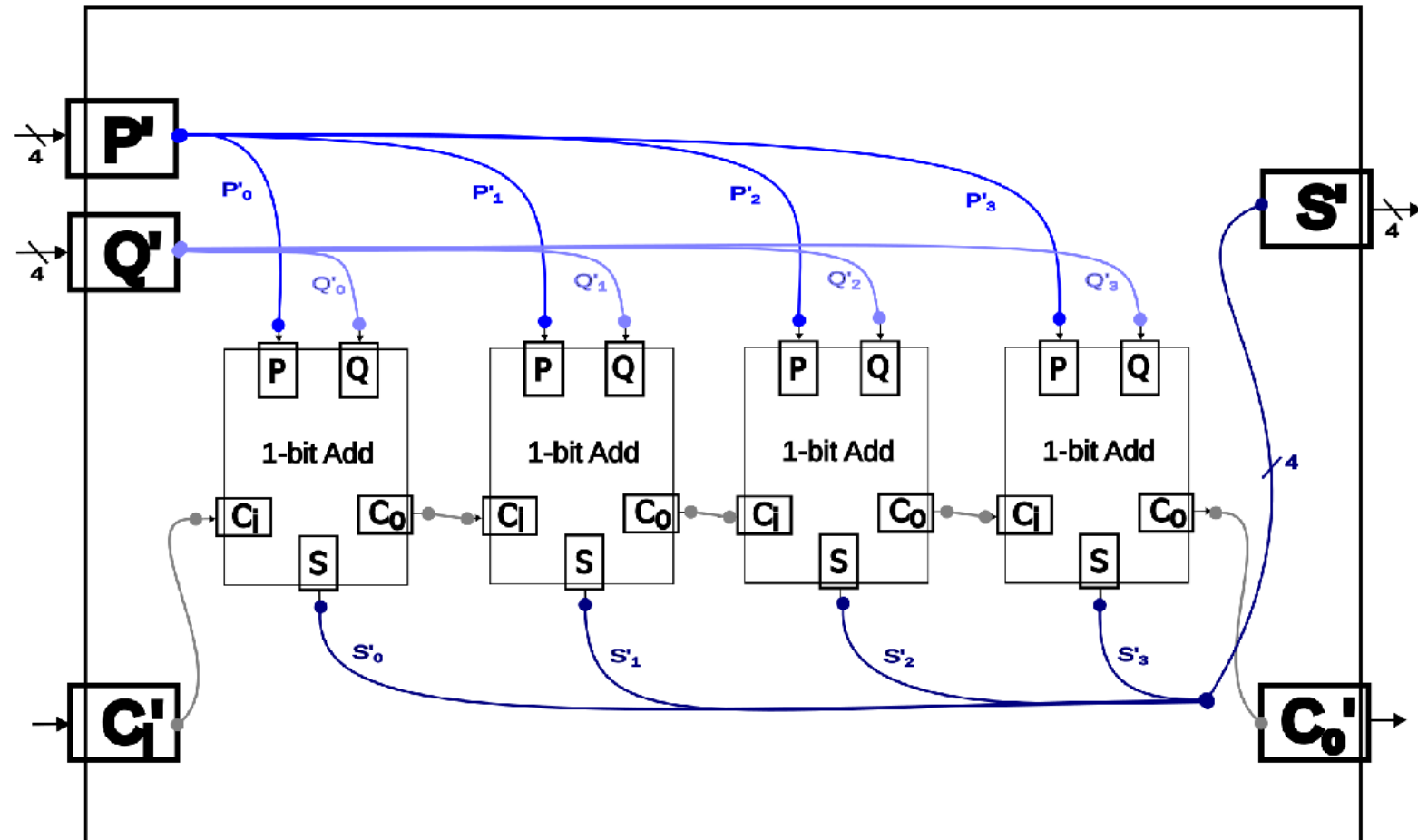



# Ripple-Carry Adder!

# Describe:

# add\_4b

```
module add_4b (iC, iP, iQ, oC, oS);  
  input iC;  
  input[3:0] iP, iQ;  
  output oC;  
  output[3:0] oS;  
  wire oC;  
  wire[3:0] oS;  
  wire[2:0] tC;  
  add_1b bit0 (iC, iP[0], iQ[0], tC[0], oS[0]);  
  add_1b bit1 (tC[0], iP[1], iQ[1], tC[1], oS[1]);  
  add_1b bit2 (tC[1], iP[2], iQ[2], tC[2], oS[2]);  
  add_1b bit3 (tC[2], iP[3], iQ[3], oC, oS[3]);  
endmodule
```

# Extra:

⇒ CLA?

Describe:


add\_4b\_tb

```

module add_4b_tb ();
reg dC;
reg[3:0] dP,dQ;
wire mC;
wire[3:0] mS;
reg cC;
reg[3:0] cS;
integer loop,ecnt;
initial begin
    ecnt=0;
    for (loop=0;loop<512;loop=loop+1) begin
        {dC,dP,dQ} = loop;
        #5;
        {cC,cS} = dP + dQ + dC;
        if (mC!==(cC||mS!==(cS)) begin
            ecnt = ecnt + 1;
        end
        #5;
    end
    if (ecnt==0) begin
        $display("-- Module add_4b verified!");
    end
    else begin
        $display("*** Module add_4b with error(s)! (%d)",ecnt);
    end
    $stop;
end
add_4b dut (dC,dP,dQ,mC,mS);
endmodule

```

# 1-bit Subtract

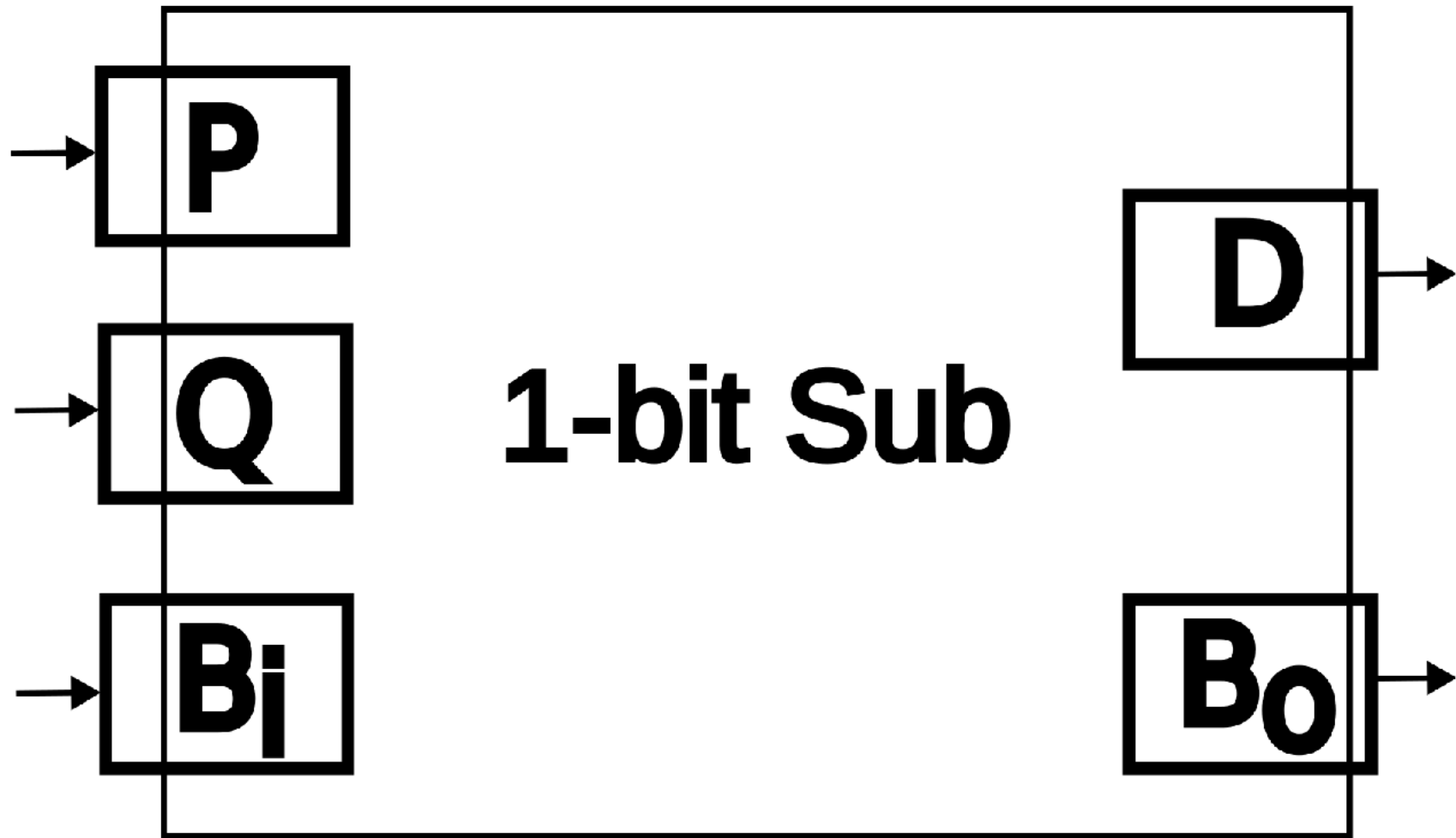



iB	iP	iQ	oB	oD
0	0	0	0	0
0	0	1	1	1
0	1	0	0	1
0	1	1	0	0
1	0	0	1	1
1	0	1	1	0
1	1	0	0	0
1	1	1	1	1

Get SOP equation!

# Homework:

⇒ sub\_1b, sub\_1b\_tb

⇒ sub\_4b, sub\_4b\_tb