

NMK20603

Computer Architecture

Codes so far:

✓ alu_4b

✓ regblock4

Processor Core

⇒ what else?

Control Logic!

⇒ sequencing

Describing (Finite) State Machine

State Machine

- ✓ mathematical model
- ✓ abstract, finite states
- ✓ states mutual exclusive

Components:

- ✓ current state (seq.)
- ✓ next state logic (comb.)
- ✓ output logic (comb.)

How to 'keep'
current state?

Still dff!

▶ different need

⇒ enb/preset/clear

Describe:

⇒ dffepc

✓ iclk, ienb

✓ ipre, iclr

✓ idat, odat

```
module dffepc (iclk, ienb, ipre, iclr, idat, odat);
input iclk, ienb, ipre, iclr;
input idat;
output odat;
reg odat;
// synchronous pre/clr
always @(posedge iclk) begin
    if (ipre===1'b1) begin
        odat = 1'b1;
    end
    else if (iclr===1'b1) begin
        odat = 1'b0;
    end
    else if (ienb===1'b1) begin
        odat = idat;
    end
end
endmodule
```

Practice:

dffepc_tb

State/Sequence:

⇒ get code

⇒ read reg

⇒ process

⇒ write reg

State Encoding

✓ binary

✓ gray

✓ 1- $\{\text{hot,cold}\}$

1-hot Encoding

⇒ Ring Counter!

✓ simpler output logic

Note: 'Covers'
next state logic!

Describe:

ringctr4

✓ iclk,irst,ienb,ostt

```
module ringctr4 (iclk,irst,ienb,ostt);  
input iclk,irst,ienb;  
output[3:0] ostt;  
wire[3:0] ostt, qout;  
dffepc s0 (iclk,ienb,irst,1'b0,qout[3],qout[0]);  
dffepc s1 (iclk,ienb,1'b0,irst,qout[0],qout[1]);  
dffepc s2 (iclk,ienb,1'b0,irst,qout[1],qout[2]);  
dffepc s3 (iclk,ienb,1'b0,irst,qout[2],qout[3]);  
assign ostt = qout;  
endmodule
```

Testbench?

Practice:

⇒ task>state_reset

```
// task to reset system
reg drst;
task state_reset ;
    input integer clen;
    integer iter;
    begin
        $write("[%05g] Reset state machine ",$time);
        $display("for %g clock cycles",clen);
        drst = 1'b1;
        for (iter=0;iter<clen;iter=iter+1) begin
            #(CLKP);
        end
        drst = 1'b0;
    end
endtask
```

Practice:

⇒ task>state_cycle

```
// task to runs single machine cycle
reg denb;
wire[3:0] mstt;
task state_cycle ;
    reg[3:0] curr;
    begin
        $display("[%05g] Running a cycle", $time);
        curr = mstt; denb = 1'b1;
        while (mstt==curr) #(CLKP);
        while (mstt!=curr) #(CLKP);
        denb = 1'b0;
        $display("[%05g] Completed cycle", $time);
    end
endtask
```

Practice:

⇒ 'monitor' code?


```
always @(mstt) begin // check changes in state
    case (mstt)
        4'b0001: $display("[%05g] STATE0", $time);
        4'b0010: $display("[%05g] STATE1", $time);
        4'b0100: $display("[%05g] STATE2", $time);
        4'b1000: $display("[%05g] STATE3", $time);
        default:
            $display("[%05g] STATEX (%04b)", $time, mstt);
    endcase
end
```

Describe:

ringctr4_tb

```
module ringctr4_tb ();
// clock generator
// task:state_reset
// task:state_cycle
// output monitor
// the rest...
initial begin
    // reset code
    dclk = 1'b1; denb = 1'b0; drst = 1'b0;
    $display("[%05g] CurrentState:%b", $time, mstt);
    #(CLKP/2) state_reset(2);
    #(CLKP);
    #(CLKP) state_cycle();
    #(CLKP);
    #(CLKP) state_cycle();
    #(CLKP);
    $finish;
end
ringctr4 dut (dclk, drst, denb, mstt);
endmodule
```

Alternative
ringctr4 code?
✓ behavioral!

```
module ringctr4bhv (iclk,irst,ienb,ostt);
input iclk,irst,ienb;
output[3:0] ostt;
reg[3:0] ostt;
always @(posedge iclk) begin
    if (irst==1'b1) begin
        ostt = 4'b0001;
    end
    else if (ienb==1'b1) begin
        case (ostt)
            4'b0001: ostt = 4'b0010;
            4'b0010: ostt = 4'b0100;
            4'b0100: ostt = 4'b1000;
            4'b1000: ostt = 4'b0001;
        endcase
    end
end
endmodule
```

Homework:

⇒ ringctr4bhv_tb