

Introduction to Verilog and ModelSim


(Part 6 – State Machines)



State Machine

- Actually, a Finite State Machine (FSM)
 - mathematical model of computation
 - abstract machine with finite states
 - can only be in ONE state at any given time
- Consists of
 - next state logic calculation (combinational)
 - current state logic (sequential)
 - output / control logic (combinational)


State Machine (cont.)

 

State Machine (cont.)

- State machines for control applications
 - 2 distinct types: Moore and Mealy machines
- Moore Machine
 - output depends only on state
 - entry actions only
- Mealy Machine
 - output depends on both state and input
 - input actions only

State Diagram

 


- Many variants
 - Use the one used here
- Circles are states
 - Actions (e.g. entry, exit) tied to states
- Arrows are transitions
 - Specify cause triggers
 - Special arrow for initial state (reset@default)

State Encoding

- Binary encoding
 - Normal binary counter (e.g. 00, 01, 10, 11)
- Gray encoding
 - Basically a counter with a single bit transition
 - (e.g. 00, 01, 11, 10)
- One-`{hot,cold}` encoding
 - Single bit 'active' at a time (hot-1,cold-0)
 - (e.g. 0001, 0010, 0100, 1000)


FSM Implementation

 - Example: Traffic Light Controller
 - L2 will be at GREEN (G), L1 at RED (R)
 - When S1 triggers → L2 changes after t_D time unit
 - L2=Y for t_Y time unit, L2=R for t_R time unit
 - L1=G for t_G time unit
 - L1=Y for t_Y time unit
 - L1=R for t_R time unit




FSM Implementation (cont.)

 - Clearly,
 - 6 output lines
 - 1 input line
- But, what about time?
 - Assume timers!
 - 4 inputs, 4 outputs



- So, target module:

 

FSM Implementation (cont.)

- Outputs and State Diagram

- $S1=\{1,0,0,0,0,1,0,0,0,0\}$

- $S2=\{1,0,0,0,0,1,0,0,0,1\}$

- $S3=\{1,0,0,0,1,0,0,1,0,0\}$


- $S4=\{1,0,0,1,0,0,1,0,0,0\}$

- $S5=\{0,0,1,1,0,0,0,0,1,0\}$

- $S6=\{0,1,0,1,0,0,0,1,0,0\}$


- $S7=\{1,0,0,1,0,0,1,0,0,0\}$

 - Is this a Mealy Machine or a Moore Machine?



FSM Implementation (cont.)

 - Decide state encoding
 - binary encoding (minimum number of register)
 - 1-hot encoding (easier to decode @ get output logic)
- Get equation for output logic
 - 1 equation per output line
 - Mealy (input & state) or Moore (state only)
- Get equation for next state logic
 - state register output(s) → input(s)
 - next state logic output → state register input



Let's choose these!

FSM Implementation (cont.)

- Truth table for output logic

cS[2]	cS[1]	cS[0]	L1	L2	TXd
0	0	1	{ 1,0,0 }	{ 0,0,1 }	{ 0,0,0,0 }
0	1	0	{ 1,0,0 }	{ 0,0,1 }	{ 0,0,0,1 }
0	1	1	{ 1,0,0 }	{ 0,1,0 }	{ 0,1,0,0 }
1	0	0	{ 1,0,0 }	{ 1,0,0 }	{ 1,0,0,0 }
1	0	1	{ 0,0,1 }	{ 1,0,0 }	{ 0,0,1,0 }
1	1	0	{ 0,1,0 }	{ 1,0,0 }	{ 0,1,0,0 }
1	1	1	{ 1,0,0 }	{ 1,0,0 }	{ 1,0,0,0 }

Logic for
L1 Red

FSM Implementation (cont.)

- Truth table for next state logic

Logic for D[2]

cS[2]	cS[1]	cS[0]	Trigger	nS[2]	nS[1]	nS[0]
0	0	1	S1	0	1	0
0	1	0	TDd	0	1	1
0	1	1	TYd	1	0	0
1	0	0	TRd	1	0	1
1	0	1	TGd	1	1	0
1	1	0	TYd	1	1	1
1	1	1	TRd	0	0	1

FSM in Verilog

```
module fsm_tlc (clk,rst,S1,TXd,
               L1,L2,TXi);

input clk, rst, S1;
input [3:0] TXd;
output [2:0] L1,L2;
output [3:0] TXi;
wire [2:0] L1,L2;
wire [3:0] TXi;
reg [2:0] cST;
wire [2:0] nST, nSTi;

always @(posedge clk or posedge rst)
begin
    if (rst) cST <= 3'b001;
    else cST <= nST;
end

// assign output L1
assign L1[2] = ~cST[2]|~(cST[1]^cST[0]);
assign L1[1] = cST[2]&cST[1]&~cST[0];
assign L1[0] = cST[2]&~cST[1]&cST[0];

// assign output L2
assign L2[2] = cST[2];
assign L2[1] = ~cST[2]&cST[1]&cST[0];
assign L2[0] = ~cST[2]&(cST[1]^cST[0]);

// assign output timer control
assign TXi[3] = cST[2]&~(cST[1]^cST[0]);
assign TXi[2] = cST[1]&(cST[2]^cST[0]);
assign TXi[1] = cST[2]&~cST[1]&cST[0];
assign TXi[0] = ~cST[2]&cST[1]&~cST[0];
```

```
// assign next state
assign nST[2] =
    (~cST[2]&cST[1]&cST[0]&TXd[1])|
    (cST[2]&~cST[1]&~cST[0]&TXd[0])|
    (cST[2]&~cST[1]&cST[0]&TXd[2])|
    (cST[2]&cST[1]&~cST[0]&TXd[1]);
assign nST[1] =
    (~cST[2]&~cST[1]&cST[0]&S1)|
    (~cST[2]&cST[1]&~cST[0]&TXd[3])|
    (cST[2]&~cST[1]&cST[0]&TXd[2])|
    (cST[2]&cST[1]&~cST[0]&TXd[1]);
assign nST[0] =
    (~cST[2]&cST[1]&~cST[0]&TXd[3])|
    (cST[2]&~cST[1]&~cST[0]&TXd[0])|
    (cST[2]&cST[1]&~cST[0]&TXd[1])|
    (cST[2]&cST[1]&cST[0]&TXd[0]);

endmodule
```



FSM in Verilog (Test Bench 1)

```
module fsm_tlc_tb ();
reg clk, rst, S1;
reg [3:0] TXd;
wire [2:0] L1,L2;
wire [3:0] TXi;
reg init;
// reset block
initial begin
    clk=1'b0; rst=1'b0; S1=1'b0;
    TXd[3]=0; TXd[2]=0;
    TXd[1]=0; TXd[0]=0; init = 0;
    // generate clock here
    forever #5 clk = ~clk;
end
// timer RED
always @(TXi[3]) begin
    if (init&TXi[3]) begin
        $display("[%g] TR Init",$time);
        #40 TXd[3] = 1'b1;
        $display("[%g] TR Done",$time);
    end
    else TXd[3] = 1'b0;
end
// timer YELLOW
always @(TXi[2]) begin
    if (init&TXi[2]) begin
        $display("[%g] TY Init",$time);
        #20 TXd[2] = 1'b1;
        $display("[%g] TY Done",$time);
    end
    else TXd[2] = 1'b0;
end
end
```

```
// timer GREEN
always @(TXi[1]) begin
    if (init&TXi[1]) begin
        $display("[%g] TG Init",$time);
        #200 TXd[1] = 1'b1;
        $display("[%g] TG Done",$time);
    end
    else TXd[1] = 1'b0;
end
// timer DELAY
always @(TXi[0]) begin
    if (init&TXi[0]) begin
        $display("[%g] TD Init",$time);
        #20 TXd[0] = 1'b1;
        $display("[%g] TD Done",$time);
    end
    else TXd[0] = 1'b0;
end
// generate reset signal
initial begin
    #50; rst = 1'b1;
    $display("[%g] RESET!",$time);
    #50; rst = 1'b0;
    init = 1'b1;
    $display("[%g] INIT!",$time);
end
end
```

```
// generate stimuli
initial begin
    #150; // wait reset done
    $display("[%g] S1 NOW!",$time);
    S1 = 1'b1; // trigger S1
    #20;
    S1 = 1'b0;
    #500; $stop;
end
// monitor block - state
always @(dut.cST)
begin
    $display("[%g] Check: [%b]",
        $time,dut.cST);
end
// monitor block - clock
always @(negedge clk)
begin
    $display("[%g] State: [%b]",
        $time,dut.cST);
end
// instantiate DUT
fsm_tlc dut (clk,rst,S1,
    TXd,L1,L2,TXi);
endmodule
```



FSM in Verilog (Analysis 1)

- Notice some events look out of place!
 - race conditions in software events
 - within same simulation time, no precedence!
- Testbench design can be improved
 - should avoid race conditions (generate stimuli earlier than processing clock edges – DONE!)
 - use system task \$strobe to propagate events towards the end of event queue (try replace \$display in timer always block)

Practical Session 6.1

- Rewrite the FSM module for the given traffic light controller using 1-hot encoding
- Verify the design using the same testbench

FSM in Verilog (Analysis 2)

- There is an easier way to do this → YAY!
 - using always block for combinational logic
 - state transitions are obvious
- The previous example is still important
 - shows that next-state decision logic IS combinational logic!
 - still, not really practical to use in real design (time to market!)

FSM in Verilog (Alt.)

```
module fsma_tlc (clk,rst,S1,TXd,  
    L1,L2,TXi);  
  
input clk, rst, S1;  
input [3:0] TXd;  
output [2:0] L1,L2;  
output [3:0] TXi;  
wire [2:0] L1,L2;  
wire [3:0] TXi;  
reg [2:0] cST, nST;  
  
// define useful parameters  
parameter [2:0] STATE1=3'b001,  
    STATE2=3'b010, STATE3=3'b011,  
    STATE4=3'b100, STATE5=3'b101,  
    STATE6=3'b110, STATE7=3'b111;  
  
// state register  
always @(posedge clk or  
    posedge rst)  
begin  
    if (rst) cST <= STATE1;  
    else cST <= nST;  
end
```

```
// get next state logic  
always @(S1 or TXd)  
begin  
    case (cST)  
        STATE1: if (S1) nST=STATE2;  
                else nST=STATE1;  
        STATE2:  
                if (TXd[0]) nST=STATE3;  
                else nST=STATE2;  
        STATE3:  
                if (TXd[2]) nST=STATE4;  
                else nST=STATE3;  
        STATE4:  
                if (TXd[3]) nST=STATE5;  
                else nST=STATE4;  
        STATE5:  
                if (TXd[1]) nST=STATE6;  
                else nST=STATE5;  
        STATE6:  
                if (TXd[2]) nST=STATE7;  
                else nST=STATE6;  
        STATE7:  
                if (TXd[3]) nST=STATE1;  
                else nST=STATE7;  
        default: nST = STATE1;  
    endcase  
end
```

```
// assign output L1  
assign L1[2] =  
    ~cST[2]|~(cST[1]^cST[0]);  
assign L1[1] =  
    cST[2]&cST[1]&~cST[0];  
assign L1[0] =  
    cST[2]&~cST[1]&cST[0];  
// assign output L2  
assign L2[2] = cST[2];  
assign L2[1] =  
    ~cST[2]&cST[1]&cST[0];  
assign L2[0] =  
    ~cST[2]&(cST[1]^cST[0]);  
// assign output timer control  
assign TXi[3] =  
    cST[2]&~(cST[1]^cST[0]);  
assign TXi[2] =  
    cST[1]&(cST[2]^cST[0]);  
assign TXi[1] =  
    cST[2]&~cST[1]&cST[0];  
assign TXi[0] =  
    ~cST[2]&cST[1]&~cST[0];  
  
endmodule
```

*That's all,
folks!*